

DESIGN OF 2-STAGE OTA.

• Technology used: TSMC / $0.18 \mu\text{m}$

• Given values:

$$V_{Tn} = 0.37 \text{ V} \quad V_{dd} = 1.8 \text{ V}$$

$$V_{Tp} = 0.39 \text{ V} \quad L_{min} = 0.18 \mu\text{m}$$

$$\mu_n C_{ox} = 230 \mu\text{A}/\text{V}^2 \quad W_{min} = 0.27 \mu\text{m}$$

$$\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$$

• Specifications:

1) DC gain $\geq 40 \text{ dB}$.

2) GBW = 20 MHz .

3) PM $\geq 60^\circ$.

4) Slew rate = $25 \text{ V}/\mu\text{sec}$.

5) $ICMR(+)$ = 1.6 V

6) $ICMR(-)$ = 0.8 V

7) $C_L = 5 \text{ pF}$.

8) Let; $L = 500 \text{ nm}$

{for all mosfets}

• For phase margin $\geq 60^\circ$.

Say: PM = 60°

$$C_c \geq 0.22 C_L$$

$$C_c \geq 0.22 \times 5$$

$$C_c \geq 1.1 \text{ pF}$$

\therefore let; $C_c = 1.2 \text{ pF}$

- Diagram:

Names of Transistors / MOSFETS:

M_{1-2} = Input differential pair.


$M_{3-4} =$ current mirror active loads.

M_0 = Input stage current Source

$m_5 = \text{stage 2 amplifier}$

M_6 = Stage 2 current Source.

M_7 = current mirror MOSFET. current: I_{ref} .
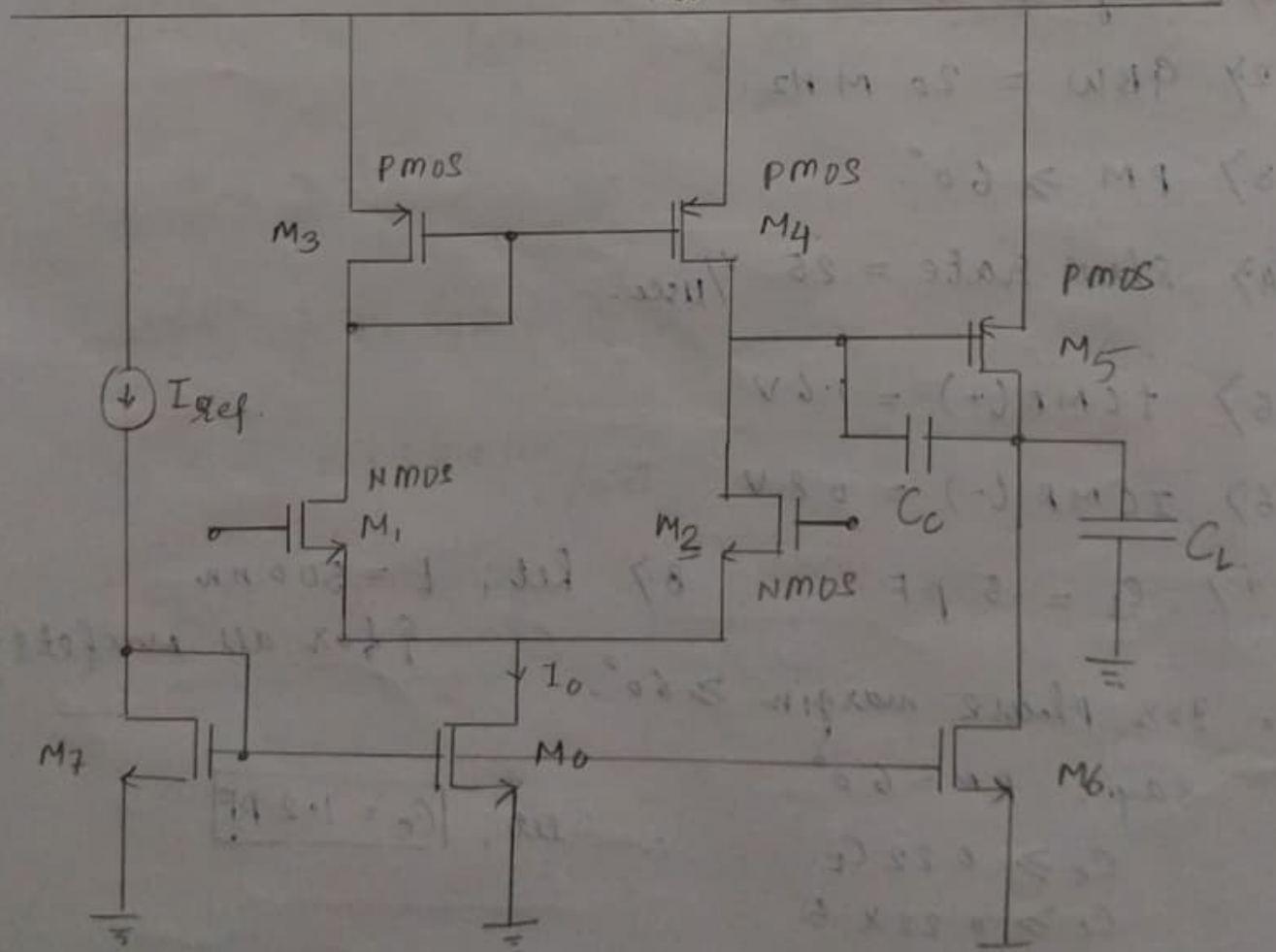
$$V_{dd} = 1.8V$$


1.7 Calculating I_0 using Slew rate:

$$S.R = \frac{I_0}{C_c}$$

$$25 \text{ V}/\mu\text{sec} = \frac{I_0}{1.2 \text{ pF}}$$

$$\boxed{I_0 = 30 \mu\text{A}}$$

2.7 Calculating M_1 and M_2 : { Using GBW }

$$\bullet g_{m1} = \text{GBW} \times 2\pi \times C_c$$

$$g_{m1} = 20 \text{ MHz} \times 2\pi \times 1.2 \text{ pF}$$

$$g_{m1} = 150.8 \mu\text{A}/\sqrt{2}$$

$$\therefore \left(\frac{\omega}{L}\right)_1 = \frac{g_{m1}^2}{4n C_{ox} \times 2 I_{D1}}$$

$$\text{here } I_{D1} = I_1$$

$$I_1 = I_0/2$$

$$\left(\frac{\omega}{L}\right)_1 = \frac{g_{m1}^2}{4n C_{ox} \times 2 I_{D1}}$$

$$I_1 = 15 \mu\text{A}$$

$$= \frac{150.8^2}{2 \times 30 \times 30}$$

$$= 3.29$$

$$\therefore \boxed{\left(\frac{\omega}{L}\right)_1 = 3.3}$$

$$\text{and } \boxed{\left(\frac{\omega}{L}\right)_2 = 3.3}$$

3) For M_3 and M_4 : { using $ICMR(+)_{\max}$ }

M_3 : always in saturation { gate and drain are connected }.


• To keep M_1 in saturation:

$$V_{D1} \geq V_g - V_{t1}$$

$$V_g \leq V_{D1} + V_{t1}$$

$$V_{in(\max)} \leq V_{D1(\min)} + V_{t1(\min)} \quad \text{--- (1)}$$

$$V_{D1} = V_{DD} - V_{sg3}$$

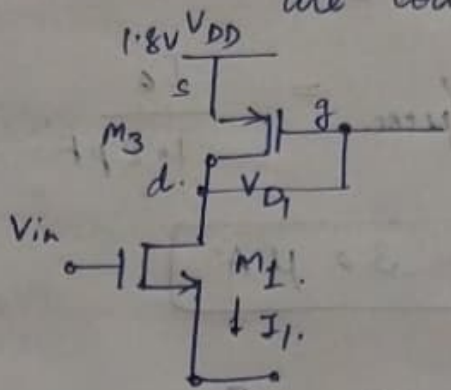

$$I_3 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_3 (\Delta V)^2 \quad \text{and } \{ I_1 = I_3 \}$$

$$I_3 = \frac{\beta}{2} (\Delta V)^2$$

$$I_3 = \frac{\beta}{2} (V_{sg} - |V_{t3}|)^2$$

$$V_{sg} = \sqrt{\frac{2I_1}{\beta}} + |V_{t3}|$$

$$\therefore V_{D1} = 1.8 - \sqrt{\frac{2I_1}{\beta}} - |V_{t3}|$$

$$\text{and } V_{in(\max)} \leq 1.8 - \sqrt{\frac{2I_3}{\beta}} - |V_{t3}| + V_{t1(\min)}$$

$$ICMR(+) = 1.8 - \sqrt{\frac{2I_3}{\beta}} - 0.39 + 0.37$$

$$1.06 = 1.8 - \sqrt{\frac{2I_3}{\mu_p C_{ox} (W/L)_3}} - 0.02$$

$$\frac{2I_3}{\mu_p C_{ox} (W/L)_3} = (0.18)^2$$

$$\left(\frac{\omega}{L}\right)_3 = \frac{2 \times 15}{100 \times (0.18)^2}$$

$$\boxed{\left(\frac{\omega}{L}\right)_3 = 9.23}$$

$$\therefore \boxed{\left(\frac{\omega}{L}\right)_4 = 9.23}$$


4) For M_0 calculation: {using ICMP(-)}

$$V_{D0} > V_{G0} - V_{tn}$$

$$V_{D0} = V_{in} - V_{GS1}$$

$$\therefore V_{D0} \geq V_{D0sat}$$

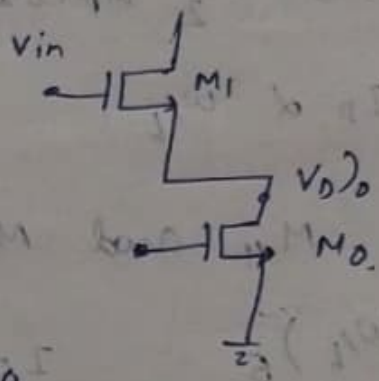value required
for keeping M_0
in saturation.



$$\therefore V_{in} \geq V_{GS1} + V_{D0sat} \Rightarrow \text{ICMP(-)} = V_{GS1}$$

$$I_{D0} = \frac{1}{2} \mu_n C_{ox} \left(\frac{\omega}{L}\right)_0 (V_{D0sat})^2$$

$$30 = \frac{1}{2} \times 230 \times \left(\frac{\omega}{L}\right)_0 \times (0.23)^2$$

$$\boxed{\left(\frac{\omega}{L}\right)_0 = 4.9}$$

$$V_{D0sat} = 0.8 - \sqrt{\frac{2I_{D1}}{\beta_1} - V_{th}}$$

$$= 0.8 - \sqrt{\frac{2 \times 15}{230 \times 3.3}} - 0.37$$

$$\boxed{V_{D0sat} = 0.23}$$

5) M_6 :

60° Phase Margin:

$$g_{m5} \geq 10 \times g_{m1}$$

$$g_{m5} \geq 10 \times 150.8$$

$$g_{m5} = 1508 \mu V_{A2}$$

$$\therefore I_D = \frac{1}{2} \mu_p C_{ox} (W/L) (V_{gs} - V_{th})^2$$

$$I_D \propto W/L$$

For M_4 and M_5 :

$$\frac{(W/L)_5}{(W/L)_4} = \frac{I_5}{I_4} = \frac{g_{m5}}{g_{m4}}$$

$$g_{m4} = \sqrt{2 \mu_p C_{ox} \left(\frac{W}{L}\right) I_D}$$

$$= \sqrt{100 \times 9.3 \times 2 \times 15}$$

$$= 167$$

$$(W/L)_5 = \frac{1508}{167} \times 9.3$$

$$(W/L)_5 = 84$$

for I_5 :

$$\frac{I_5}{I_4} = \frac{(w/L)_5}{(w/L)_4}$$

$$I_5 = \frac{84}{9.23} \times 15$$

$$\boxed{I_5 = 136.5 \mu A} \quad \left. \vphantom{\boxed{I_5 = 136.5 \mu A}} \right\} \text{stage 2 current}$$

$$\text{and } \frac{I_6}{I_0} = \frac{(w/L)_6}{(w/L)_0} \quad \left. \vphantom{\frac{I_6}{I_0} = \frac{(w/L)_6}{(w/L)_0}} \right\} \text{lower current sources.}$$

$$(w/L)_6 = \frac{136.5}{30} \times 4.9$$

$$\boxed{(w/L)_6 = 22.3 \mu m}$$

$$6) I_{ref} = \frac{1}{10} I_0$$

$$= \frac{1}{10} \times 30 \mu A = 3 \mu A$$

$$\therefore (w/L)_7 = \frac{1}{10} \times (w/L)_0$$

$$(w/L)_7 = \frac{1}{10} \times 4.9$$

$$\boxed{(w/L)_7 = 0.49}$$

a)

MOSFET	(W/L)	L	W
M ₁₋₂	3.3	500 nm	1650 nm
M ₃₋₄	9.23	500 nm	4615 nm
M ₅	84.7	500 nm	42000 nm
M ₆	22.3	500 nm	11150 nm
M ₀	4.9	500 nm	2450 nm
M ₇	0.49	1500 nm	490 490 nm

b) Power Drawn: current drawn $\times V_{supply}$.

$$\Rightarrow (I_7 + I_0 + I_6) \times V_{DD}$$

$$\Rightarrow (30 + 136.5 + 3) \mu A \times 1.8$$

$$\Rightarrow 305.1 \mu W$$

$$\Rightarrow 0.305 mW.$$

c) DC gain:

Net gain: 76 dB.

Stage 1 (Differential Stage): 41.2 dB.